

MCQS

Question 1: What is the output of an OR gate if the inputs are 1 and 0?		✓
0		
1		
OFF		
2		
Question 2: What is the output of an AND gate if the inputs are 1 and 0?		✓
ON		
2		
1		
0		
Question 3: What is the output of a NOT gate if the inputs is 0?		✓
1		
0		
OFF		
2		
Question 4: A NOT gate has...		✓
Two inputs and one output		
One input and one output		
One input and two outputs		
Two inputs and two outputs		
Question 5: An OR gate has		✓
Two inputs and one output		
One input and one output		
One input and two outputs		
Two inputs and two outputs		
Question 6: The output of any logic gate can have either of two _____ ?		✓
Gates		
States		
Inputs		
Outputs		
Question 7: A logic state can only be....		✓
On or 1		
Off or 1		
1 or 0		
In and Out		

MCQS

Question 8: The output of a _____ gate is only 1 when both inputs are 1.		✓
OR		
NOT		
NAND		
AND		
Question 9: A NAND gate is the combination of which two gates		✓
OR and AND		
AND and NOT		
NOT and OR		
OR and NAND		
Question 10: A Half-Adder circuit is...		✓
Half of an AND gate		
Half of a NAND gate		
An OR gate and a NOT gate		
A circuit to add two bits together		

MCQS ANSWERS

Question 1: What is the output of an OR gate if the inputs are 1 and 0?	✓
0	
1	
OFF	
2	
Question 2: What is the output of an AND gate if the inputs are 1 and 0?	✓
ON	
2	
1	
0	
Question 3: What is the output of a NOT gate if the inputs is 0?	✓
1	
0	
OFF	
2	
Question 4: A NOT gate has...	✓
Two inputs and one output	
One input and one output	
One input and two outputs	
Two inputs and two outputs	
Question 5: An OR gate has	✓
Two inputs and one output	
One input and one output	
One input and two outputs	
Two inputs and two outputs	
Question 6: The output of any logic gate can have either of two _____ ?	✓
Gates	
States	
Inputs	
Outputs	
Question 7: A logic state can only be....	✓
On or 1	
Off or 1	
1 or 0	
In and Out	

MCQS ANSWERS

Question 8: The output of a _____ gate is only 1 when both inputs are 1.	✓
OR	
NOT	
NAND	
AND	
Question 9: A NAND gate is the combination of which two gates	✓
OR and AND	
AND and NOT	
NOT and OR	
OR and NAND	
Question 10: A Half-Adder circuit is...	✓
Half of an AND gate	
Half of a NAND gate	
An OR gate and a NOT gate	
A circuit to add two bits together	

We'd like to know your view on the resources we produce. By clicking on 'Like' or 'Dislike' you can help us to ensure that our resources work for you. When the email template pops up please add additional comments if you wish and then just click 'Send'. Thank you.

If you do not currently offer this OCR qualification but would like to do so, please complete the Expression of Interest Form which can be found here: www.ocr.org.uk/expression-of-interest

OCR Resources: the small print

OCR's resources are provided to support the teaching of OCR specifications, but in no way constitute an endorsed teaching method that is required by the Board and the decision to use them lies with the individual teacher. Whilst every effort is made to ensure the accuracy of the content, OCR cannot be held responsible for any errors or omissions within these resources. We update our resources on a regular basis, so please check the OCR website to ensure you have the most up to date version.

© OCR 2016 - This resource may be freely copied and distributed, as long as the OCR logo and this message remain intact and OCR is acknowledged as the originator of this work.

OCR acknowledges the use of the following content: n/a

Please get in touch if you want to discuss the accessibility of resources we offer to support delivery of our qualifications: resources.feedback@ocr.org.uk